



Schemă de principiu – Laborator nr. 4 - „Convertor c.c. – c.c. coborâtor”  
 (eng. „D.C. – D.C. step – down buck converter”)